



# **4 Bit Arithmetic and Logical Unit**

## **DE Lab Project Report**

**Submitted By**

**Ketan Gupta – 18BCS4052**

**Nandini Gaur – 18BCS4051**

**Abhishek Singh – 18BCS4050**

**Under the Guidance of**

**Mr. Anshul Sharma**

**Mr. Divneet Singh Kapoor**

**Mr. Khushal Thakur**

**Assistant Professors, Academic Unit – 1**



**Academic Unit-1**

**Chandigarh University**



## Table of Contents

1. Problem Identification .....	1
2. Features.....	2
3. Design Flow .....	3
4. Outcome .....	4
5. Cost Analysis .....	6
7. Product Catalogue .....	7



# 1. Problem Identification

---

Performing different arithmetic and logical operations (Addition, Subtraction, And, Or, Nand, Nor ) using IC's and mux for a 4 bit signal.

## 2. Features


---

- 1) Performs different type of operations:-
    - a) Addition
    - b) Substaction
    - c) And
    - d) Or
    - e) Nand
    - f) Nor
  - 2) Operation can be performed on a 4 bit signal.
  - 3) Two different signals are inputted from 8 switches.
  - 4) Selections can be made using 3 different switches.
  - 5) Output is performed in from of LED.
-




### 3. Design Flow

#### Block Diagram

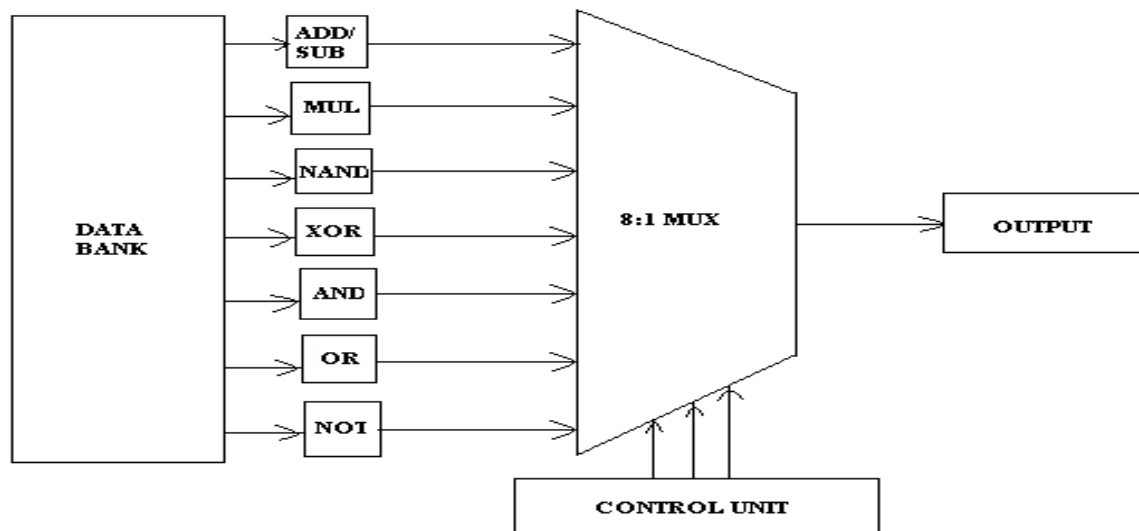

#### Circuit Diagram

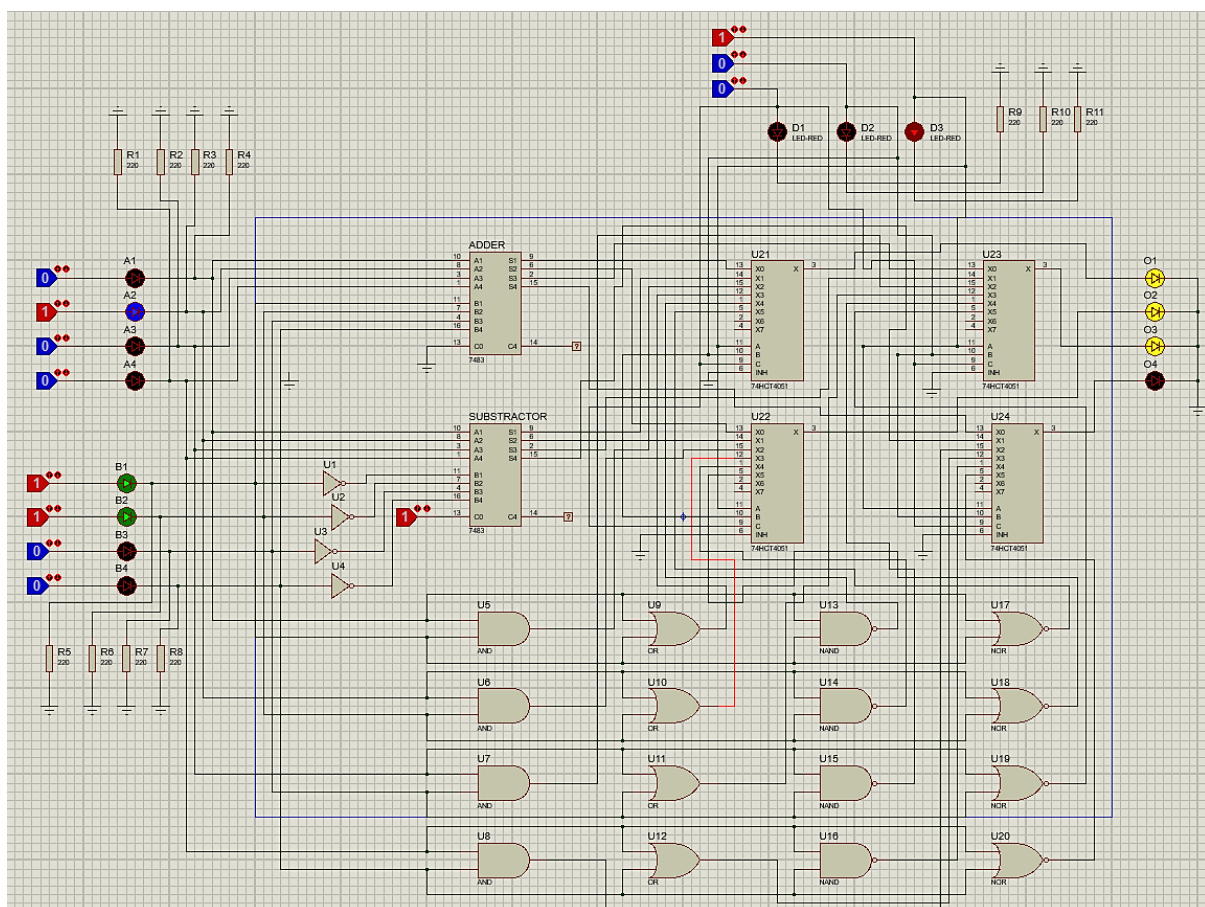



## **Materials**

<b><u>COMPONENT</u></b>	<b><u>QUANTITY</u></b>	<b><u>SPECIFICATION</u></b>
7400	1	QUAD 2-input Nand gate
7402	1	QUAD 2-input Nor gate
7404	1	Hex Inverter
7408	1	QUAD 2-input And gate
7432	1	QUAD 2-input Or gate
7483	2	4-BIT BINARY FULL ADDER
CD4051	4	Single 8-Channel Analog Multiplexer
SWITCH	12	switch
LED	15	Red, yellow and green led
BATTERY	1	9 v battery




## 4. Outcome


---

### Steps of Circuit Completion

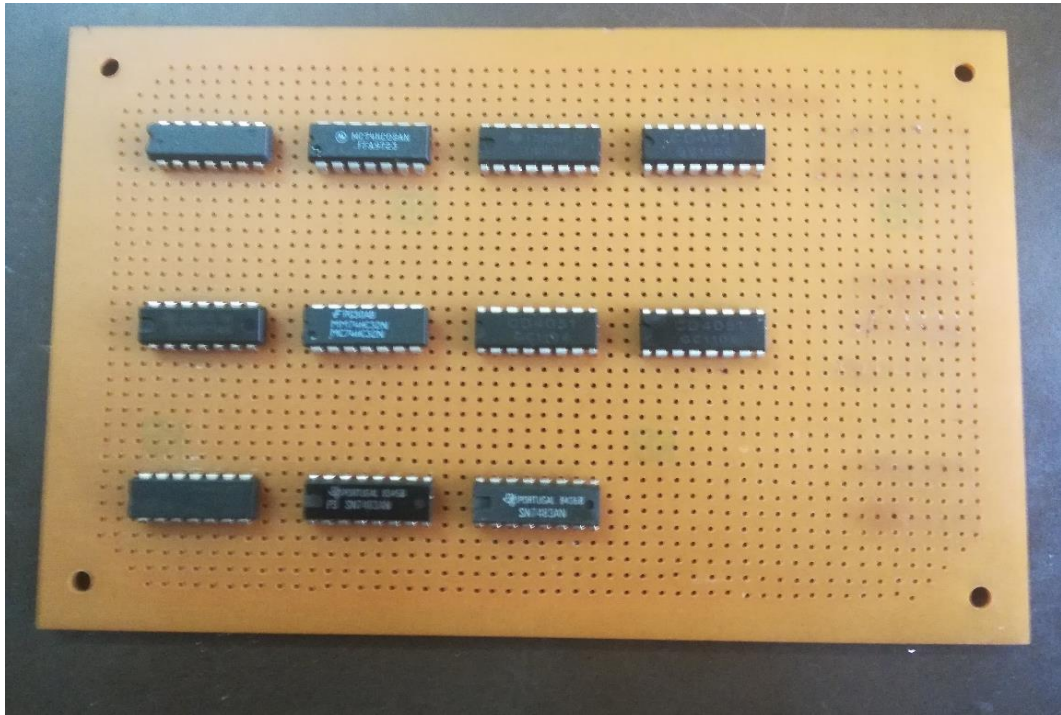- 1) IC's were connected on PCB and each terminal was soldered,



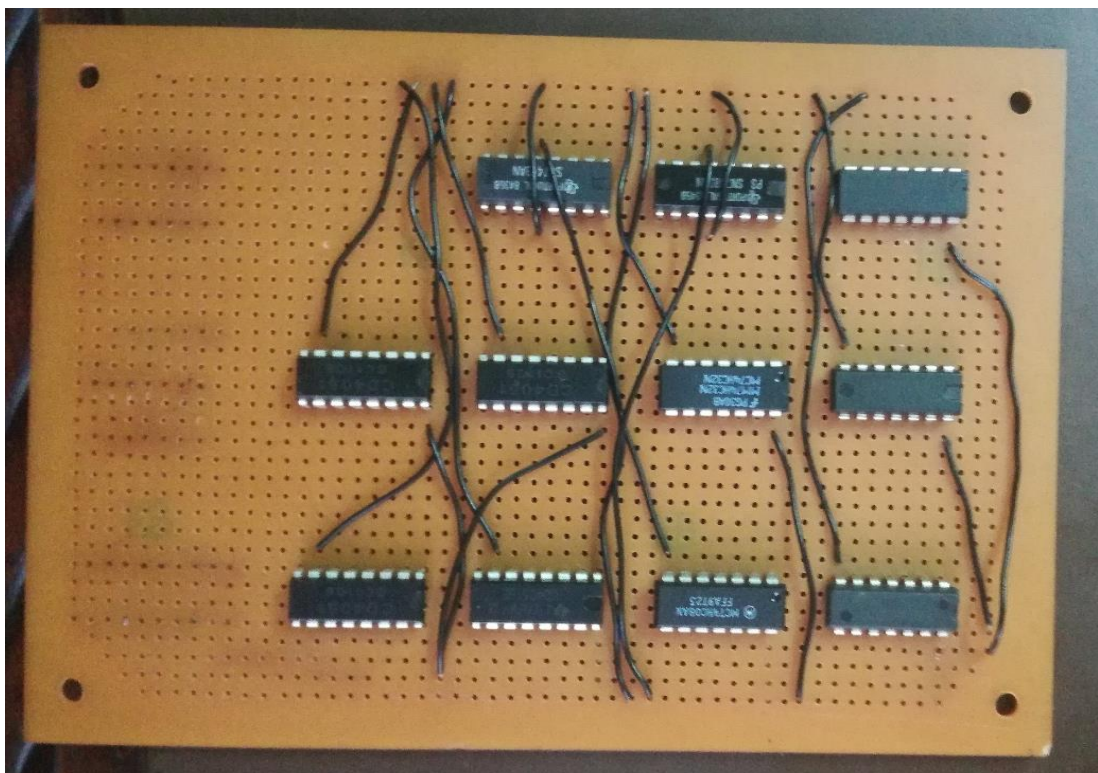
- 2) Soldering was done and IC's were powered by connect gnd and vcc;







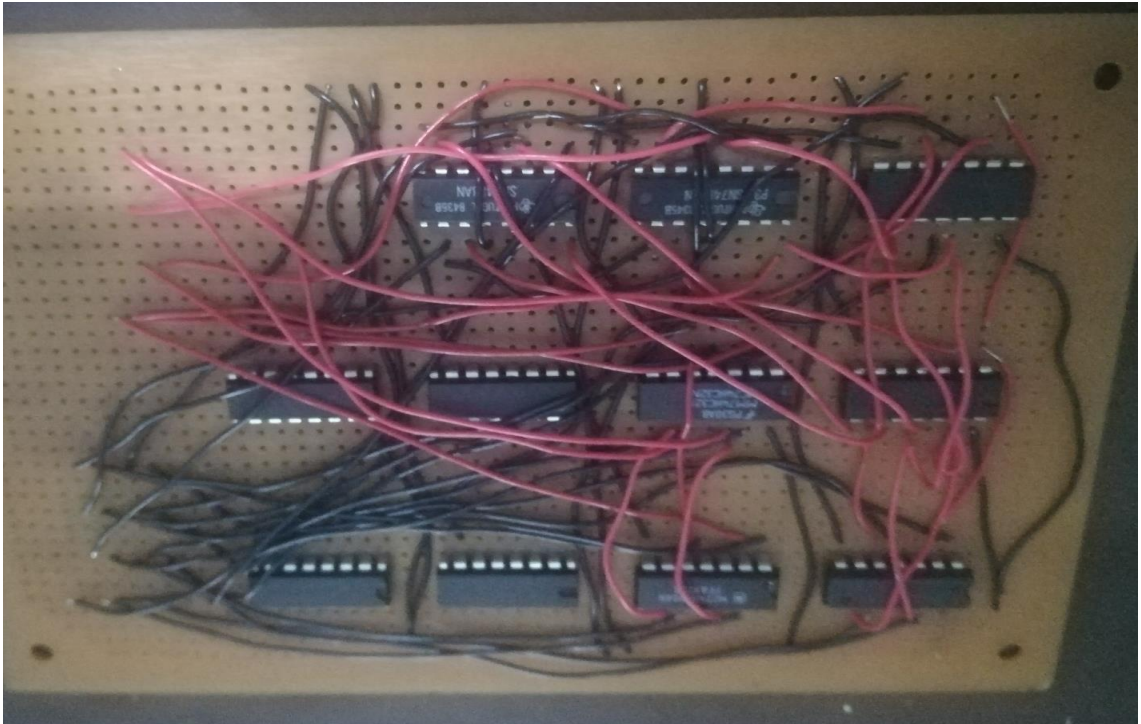- 3) Wires containing Signal A and Signal B was soldered to every IC.



- 4) Led panel was make along with switch and n/off switch.





## 5. Cost Analysis

---

S. No.	Component / Material	Price (in Rs.)
1.	7400	15 * 1
2.	7402	15 * 1
3.	7404	20 * 1
4.	7408	20 * 1
5.	7432	20 * 1
6.	7483	120 * 2
7.	4051	70 * 4
8.	PCB	50 * 1
9.	Switch	10 * 12
10.	led	1 * 20
<b>Total</b>		780/-